

***Proiect CID:***

***Proiectarea unui Automat de Tranziii  
folosind un numărător, utilizând MUX  
8:1***

***Proiect realizat de  
Mandache Stefan , grupa 2124 , semigrupa 2***

*Rezolvarea pe hartie a temei . pag 3-4*

*Testarea circuitului combinational . pag 5*

*Circuitul combinational . pag 6*

*Simularea circuitului combinational . pag 7-8*

*Testare numarator . pag 9*

*Numarator pe 3 Biti . pag 10*

*Simulare Numaratorului . pag 11*


*Implementarea in vivado cu ajutorul limbajului de programare VHDL . pag 10*

***Rezolvarea pe hartie a temei si desenele pentru  
MUX si NUMARATOR***
 
# Proiect C15

Trandade Stefan  
grupa 2124, 192  
Sesiua A.

- Implementare cu 100x 8:1
- Implementare 100x: Instruțiuni consecutive With.
- Automat: 21




U:

λ	clk	Ed	En	Action
1	X	X	X	Reset
0	↓	1	X	Load
0	↓	0	0	Count
otherwise				Wait


Gc	Gb	Ga	action	LD	PT	C	B	A
0	0	0	↑	X	X	X	X	X
0	0	1	↑	1	X	1	0	0
0	1	0	↑	1	X	0	0	1
0	1	1	↑	1	X	1	0	1
1	0	0	↑	1	X	1	1	0
1	0	1	↑	1	X	0	1	0
1	1	0	m	0	0	X	X	X
1	1	1	↑	1	X	0	1	1

LD-PT

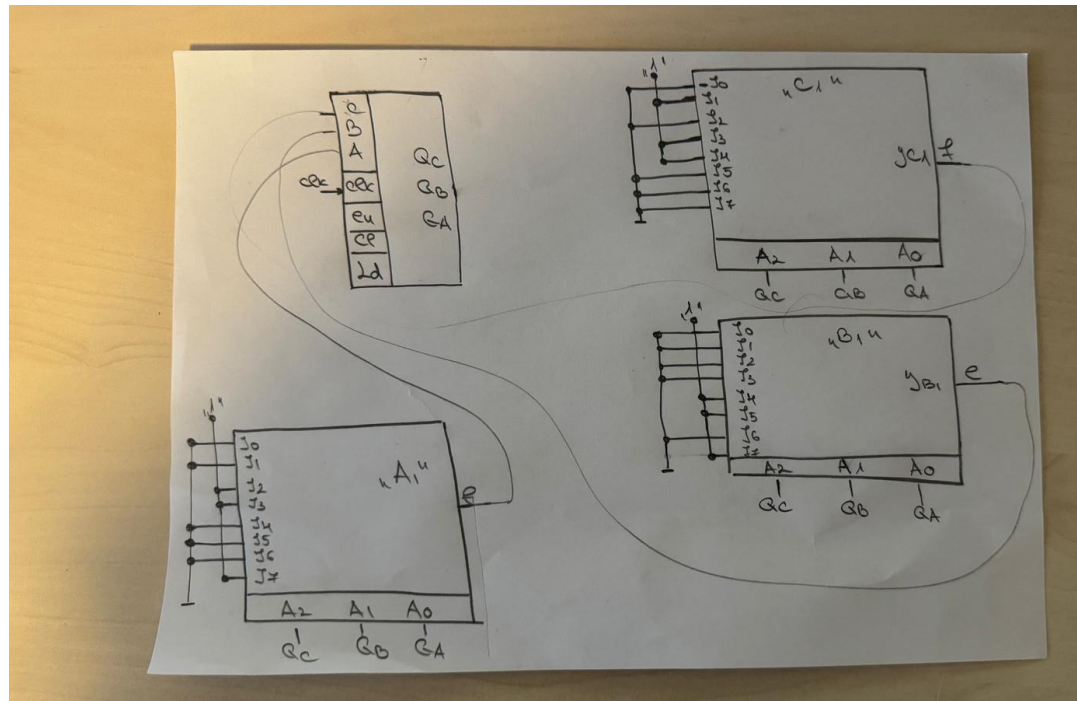X-urile pot fi activate cu 0 pentru a face calculabile.



***Testarea MUX-ului 8:1 ;***

 

*Circuit Combinational MUX 8:1 ;*

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using...

entity MUX_8_1 is
    Port ( i0 : in STD_LOGIC;
           i1 : in STD_LOGIC;
           i2 : in STD_LOGIC;
           i3 : in STD_LOGIC;
           i4 : in STD_LOGIC;
           i5 : in STD_LOGIC;
           i6 : in STD_LOGIC;
           i7 : in STD_LOGIC;
           a2 : in STD_LOGIC;
           a1 : in STD_LOGIC;
           a0 : in STD_LOGIC;
           y : out STD_LOGIC);
end MUX_8_1;

architecture Behavioral of MUX_8_1 is

    signal a :std_logic_vector(2 downto 0);

begin
    a<=a2 & a1 & a0;
    with a select

        Y <= i0 when "000",
              i1 when "001",
              i2 when "010",
              i3 when "011",
              i4 when "100",
              i5 when "101",
              i6 when "110",
              i7 when others;

end Behavioral;

```

***Simulare MUX 8:1:***

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity sim_MUX_8_1 is
  -- Port ( );
end sim_MUX_8_1;

architecture Behavioral of sim_MUX_8_1 is
  component MUX_8_1 is
    Port ( i0 : in STD_LOGIC;
           i1 : in STD_LOGIC;
           i2 : in STD_LOGIC;
           i3 : in STD_LOGIC;
           i4 : in STD_LOGIC;
           i5 : in STD_LOGIC;
           i6 : in STD_LOGIC;
           i7 : in STD_LOGIC;
           a2 : in STD_LOGIC;
           a1 : in STD_LOGIC;
           a0 : in STD_LOGIC;
           y : out STD_LOGIC);
  end component MUX_8_1;

  signal i0,i1,i2,i3,i4,i5,i6,i7,a2,a1,a0,y:std_logic;

begin
  UT: MUX_8_1 port map (i0 => i0, i1 => i1, i2 => i2, i3 => i3, i4 => i4, i5 => i5, i6 => i6, i7 => i7, a2 => a2, a1 => a1, a0 => a0, y => y);

  process
  begin
    i0<='0'; wait for 2ns;
    i0<='1'; wait for 2ns;
  end process;

  process
  begin
    i1<='0'; wait for 4ns;
    i1<='1'; wait for 4ns;
  end process;

```

```

process
begin
i2<='0'; wait for 5ns;
i2<='1'; wait for 5ns;
end process;

process
begin
i3<='0'; wait for 10ns;
i3<='1'; wait for 10ns;
end process;

process
begin
i4<='0'; wait for 15ns;
i4<='1'; wait for 15ns;
end process;

process
begin
i5<='0'; wait for 20ns;
i5<='1'; wait for 20ns;
end process;

process
begin
i6<='0'; wait for 25ns;
i6<='1'; wait for 25ns;
end process;

process
begin
i7<='0'; wait for 30ns;
i7<='1'; wait for 30ns;
end process;

| process
| begin
| a2<='0'; wait for 35ns;
| a2<='1'; wait for 35ns;
| end process;

| process
| begin
| a1<='0'; wait for 40ns;
| a1<='1'; wait for 40ns;
| end process;


| process
| begin
| a0<='0'; wait for 45ns;
| a0<='1'; wait for 45ns;
| end process;

| end Behavioral;

```



*Testare Numarator :*

 

## *Numarator pe 3 Biti :*

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
-- Uncomment the following library declaration if using...

entity NUM1 is
    Port ( d : in STD_LOGIC_VECTOR (2 downto 0);
          clk : in STD_LOGIC;
          r : in STD_LOGIC;
          en : in STD_LOGIC;
          ld : in STD_LOGIC;
          q : out STD_LOGIC_VECTOR (2 downto 0));
end NUM1;

architecture Behavioral of NUM1 is
    signal qint : STD_LOGIC_VECTOR(2 downto 0) := "011";
begin
    process(clk, r)
    begin
        if r = '1' then
            qint <= "011";
        elsif rising_edge(clk) then
            if ld = '0' then
                qint <= d;
            elsif ld = '1' and en = '1' then
                qint<=qint+1;
            else
                qint <= qint;
            end if;
        end if;
    end process;

    q <= qint;
end Behavioral;
```

## *Simulare Numaratorului :*

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

] -- Uncomment the following library declaration if using...

] entity sim_num is
  -- Port ( );
] end sim_num;

] architecture Behavioral of sim_num is
] component Project is
  Port ( clk : in STD_LOGIC;
        r : in STD_LOGIC;
        en : in STD_LOGIC;
        ld : in STD_LOGIC;
        q : out STD_LOGIC_VECTOR (2 downto 0));
] end component Project;
  signal clk,r,en,ld:std_logic;
  signal q: std_logic_vector(2 downto 0);
  begin
] UUT : Project port map (clk=>clk,
  r=>r,
  en=>en,
  ld=>ld,
] q=>q);
  r<='0' after 0ns,
  '1' after 15 ns,
  '0' after 20 ns,
  '1' after 35 ns,
  '0' after 40 ns,
  '1' after 55ns;

  ld<='1' after 0ns;
  en<='1'after 0ns;
] process
  begin
    clk<='0' ; wait for 1ns;
    clk<='1' ; wait for 1ns;
] end process;
```

## *Implementarea in vivado cu ajutorul limbajului de programare VHDL:*

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

] -- Uncomment the following library declaration if using...

] entity sim_num is
  -- Port ( );
] end sim_num;

] architecture Behavioral of sim_num is
] component Proiect is
  Port ( clk : in STD_LOGIC;
        r : in STD_LOGIC;
        en : in STD_LOGIC;
        ld : in STD_LOGIC;
        q : out STD_LOGIC_VECTOR (2 downto 0));
] end component Proiect;
  signal clk,r,en,ld:std_logic;
  signal q: std_logic_vector(2 downto 0);
  begin
] UUT : Proiect port map (clk=>clk,
  r=>r,
  en=>en,
  ld=>ld,
] q=>q);
  r<='0' after 0ns,
  '1' after 15 ns,
  '0' after 20 ns,
  '1' after 35 ns,
  '0' after 40 ns,
  '1' after 55ns;

  ld<='1' after 0ns;
  en<='1'after 0ns;
] process
  begin
    clk<='0' ; wait for 1ns;
    clk<='1' ; wait for 1ns;
] end process;
```